

# Faculty of Computing

Year 1 Semester 1 (2024)

IIT1140 – Fundamental of Computing

Lab Sheet 04


---

## Objectives:

1. To understand the behavior of Adder circuits.
  2. To understand the design of Adder circuits and multiplexers.
- 

## Activity 01:

- a) Design the following circuit in MM Logic and write the truth table. Copy your answer to the submission file.

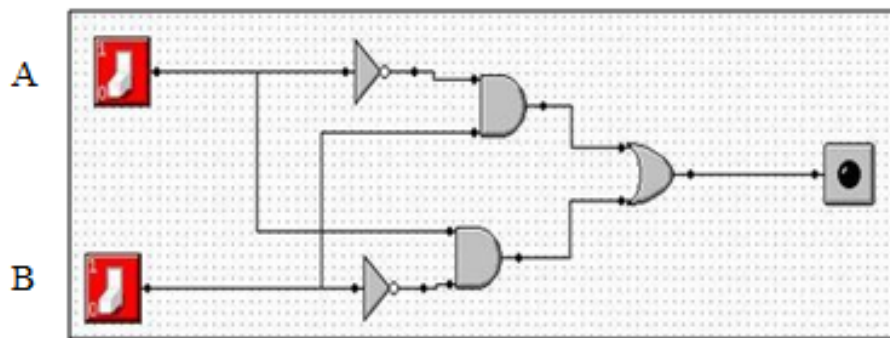

*Figure 4.1*

- b) Draw the circuit for P XOR Q and write the truth table for them.
- c) What is the similarity between the XOR circuit, and the circuit designed in (a) ?

### Activity 02:

- Design the circuits given in figure 4.2 and 4.3 in MM Logic. Copy your file to the submission file.
- Identify the names of the circuits designed in (a) and list the purpose of them.

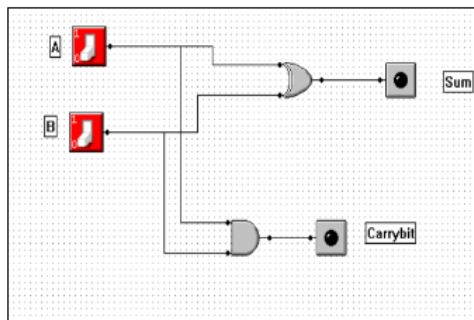


Figure 4.2

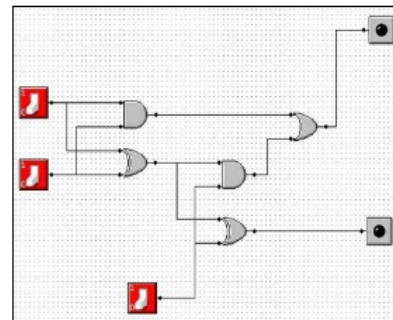


Figure 4.3

### Activity 03:

A multiplexer (or MUX) is a device that combines several analog or digital input signals and forwards them into a single output line. A multiplexer of  $2n$  inputs has  $n$  select lines, which are used to select which input line to send to the output.

- Design the following MUX circuit in MM Logic and observe its behavior

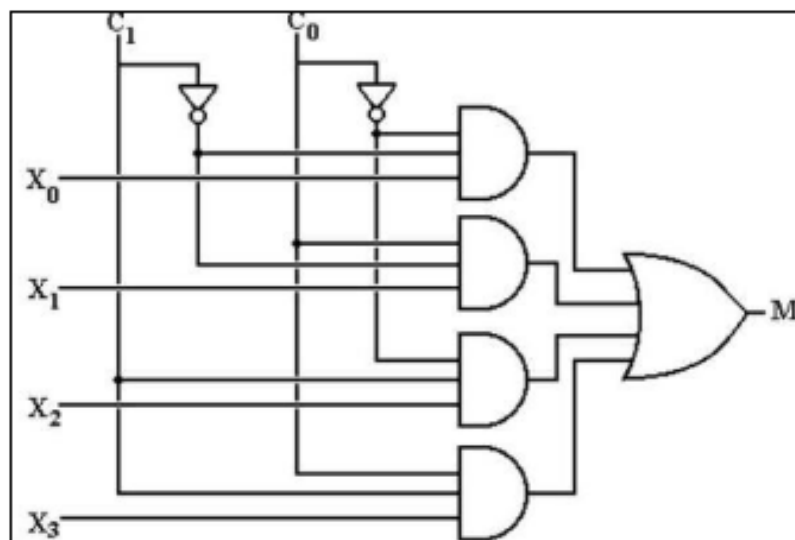


Figure 4.4